



K23U 1111

Reg. No. :

Name :

**IV Semester B.Sc. Degree (CBCSS – OBE – Regular/Supplementary/
Improvement) Examination, April 2023
(2019 Admission Onwards)**

**GENERAL AWARENESS COURSE IN COMPUTER SCIENCE
4A13CSC : Digital Electronics**

Time : 3 Hours

Max. Marks : 40

**PART – A
(Short Answer)**

Answer **all** questions :

(6×1=6)

1. What is a Digital system ?
2. List any four number systems.
3. Convert 329 to binary.
4. Which are the basic gates used in digital systems ?
5. State distributive and associative laws of algebra.
6. Write a note on XOR gate.

**PART – B
(Short Essay)**

Answer **any six** questions :

(6×2=12)

7. Explain Excess 3 code.
8. Compute the binary equivalent of $(5C7)_{16}$.
9. Explain about SOP form.
10. Realize the XOR function using AOI logic.

P.T.O.



11. What are combinational circuits ? Explain.
12. Explain about full adder.
13. What is a latch ? How is it differ from a flip flop ?
14. What are shift registers ?

PART – C
(Essay)

Answer **any four** questions :

(4×3=12)

15. Explain about BCD, GRAY code and UNICODE.
16. Briefly explain about K map.
17. Write the universal properties of NAND gates.
18. Differentiate decoders and encoders.
19. Explain the working of a SR flip flop.
20. Explain the design of a synchronous counter.

PART – D
(Long Essay)

Answer **any two** questions :

(2×5=10)

21. What is a number system ? Explain different number systems.
 22. State and prove De-Morgan's theorems.
 23. Illustrate the design of multiplexers and de-multiplexers.
 24. Explain the working of a Master Slave Flip Flop.
-