

Reg.	No.	 			ge 1 fc	W.a	inoii			
Name	e :	 	*	*						V

V Semester B.Sc. Degree (CCSS-Reg./Supple./Imp.) Examination, November 2015 CORE COURSE IN COMPUTER SCIENCE 5B11 CSC(E06) : Digital Systems and Microprocessors (Elective)

Time : 3 Hours

Max. Weightage: 21

Instructions : Section A : Answer all questions. Section B : Answer any five – Weightage 1 for each question. Section C : Answer any five – Weightage 2 for each question. Section D : Answer any one – Weightage 4.

SECTION-A

Answer all question. Weightage for a bunch of 4 questions is 1. ()

- 1. Given any logic circuit with NOR gates, one can replace it with a bubbled ______gate.
- 2. _____ is a visual display of SOP solution. We bus autonomously and ted W . ds
- 3. If the inputs to a BCD to decimal decoder is 1010 the output will be _____
- 4. _____ is an example of asynchronous counter. ______ is an example of asynchronous counter. _______ is
- 5. Physical address in 8086 has _____ bits.
- 6. Interrupt INTR can be masked using _____ bit in PSW.
- 7. 8255 has _____ programmable I/O pin connections.
- 8. How many 8259A IC are required to have 64 interrupt inputs ? (W =1)

26. What is 8254 ? Discuss its various operating modes and areas of applications

P.T.O.

M 9778

M 9778

SECTION-B

Answer any five questions. Weightage 1 for each.

- 9. What is a logic gate ?
- 10. State the associative property of Boolean algebra.
- 11. Mention two uses of decoder.
- 12. Define race around condition.
- 13. How many interrupt lines does 8086 have ? What do they do ?
- 14. What is the purpose of MN/MX pin?
- 15. What is priority resolver ?
- 16. What is the advantage of using DMA in data transfer?

(5×1=5)

not caup to server the participant SECTION - C and Security 2

Answer any five questions. Weightage 2 for each.

- 17. Differentiate a demultiplexer and a decoder on the basis of their design and function.
- 18. Draw the logic circuit for

 $Y = (\overline{A} + B + C) (A + B + \overline{C})$. So the density of the state of t

Use Boolean algebra to simplify the equation. Then draw the corresponding logic circuit.

- 19. How an SR flip-flop can be converted to J-K flip-flop?
- 20. What are synchronous and asynchronous counters ?
- 21. Explain the functions of various registers in 8086.
- 22. Why 8086 uses 20 bit address bus ? How I/O devices are addressed ?
- 23. What are the addressing modes of 8086 ? Explain.
- 24. How 8255 IC act as a peripheral interface with 8086 microprocessor? (5×2=10)

SECTION - D

Answer any one question. Weightage 4 for each.

- 25. a) What is propagation delay ? How it affects the digital circuits ?
- b) With neat diagrams explain mod-3 counter.
- 26. What is 8254 ? Discuss its various operating modes and areas of applications.

 $(1 \times 4 = 4)$